

Digital Logic Design + Computer Architecture


Sayandeep Saha

Assistant Professor
Department of Computer
Science and Engineering
Indian Institute of Technology
Bombay



Combinational Circuits

Do You Want to Design Some Day?

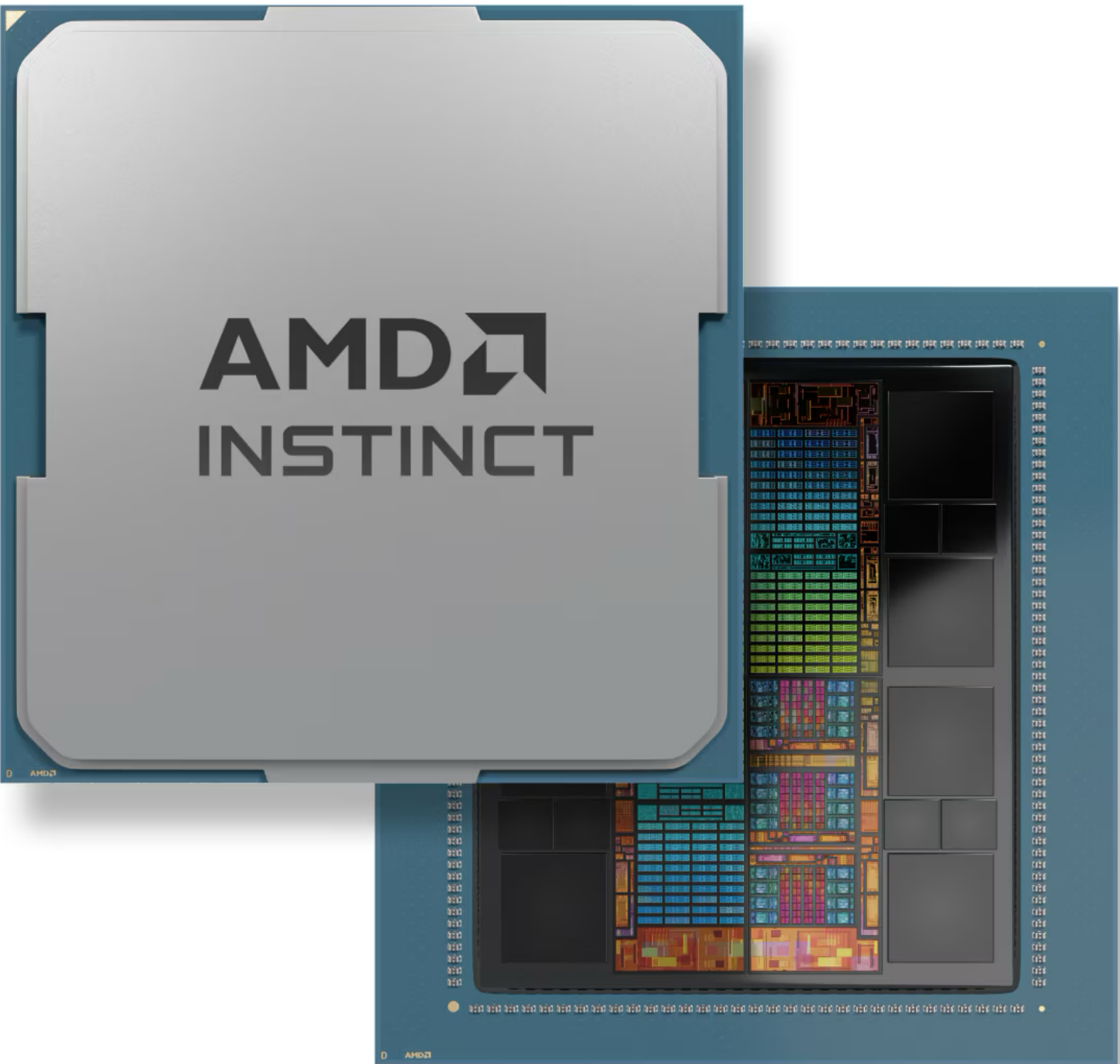

Design with Gates

- **Logic gates:** perform logical operations on input signals
- **Positive (negative) logic polarity:** constant 1 (0) denotes a high voltage and constant 0 a low (high) voltage
- **Combinational circuits:** No memorization
- **Synchronous sequential circuits:** have memory; driven by a clock that produces a train of equally spaced pulses
- **Propagation delay:** time to propagate a signal through a gate
- **Asynchronous circuits:** are almost free-running and do not depend on a clock; controlled by initiation and completion signals

Exclusive-OR (XOR) and XNOR

Exclusive-OR: modulo-2 addition, i.e., $A \oplus B = 1$ if either A or B is 1, but not both.

Commutativity: $A \oplus B = B \oplus A$

Associativity: $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$

Distributivity: $(AB) \oplus (AC) = A(B \oplus C)$

If $A \oplus B = C$, then

$$A \oplus C = B$$

$$B \oplus C = A$$

$$A \oplus B \oplus C = 0$$

Exclusive-OR of an even (odd) number of elements, whose value is 1, is 0 (1)


XNOR: Complement of XOR

Combinational Circuits: Parity-bit Generator

Parity-bit generator: produces output value 1 if and only if an odd number of its inputs have value 1

xy		z			
		00	01	11	10
z	0	0	1	0	1
	1	1	0	1	0

(a) Map.

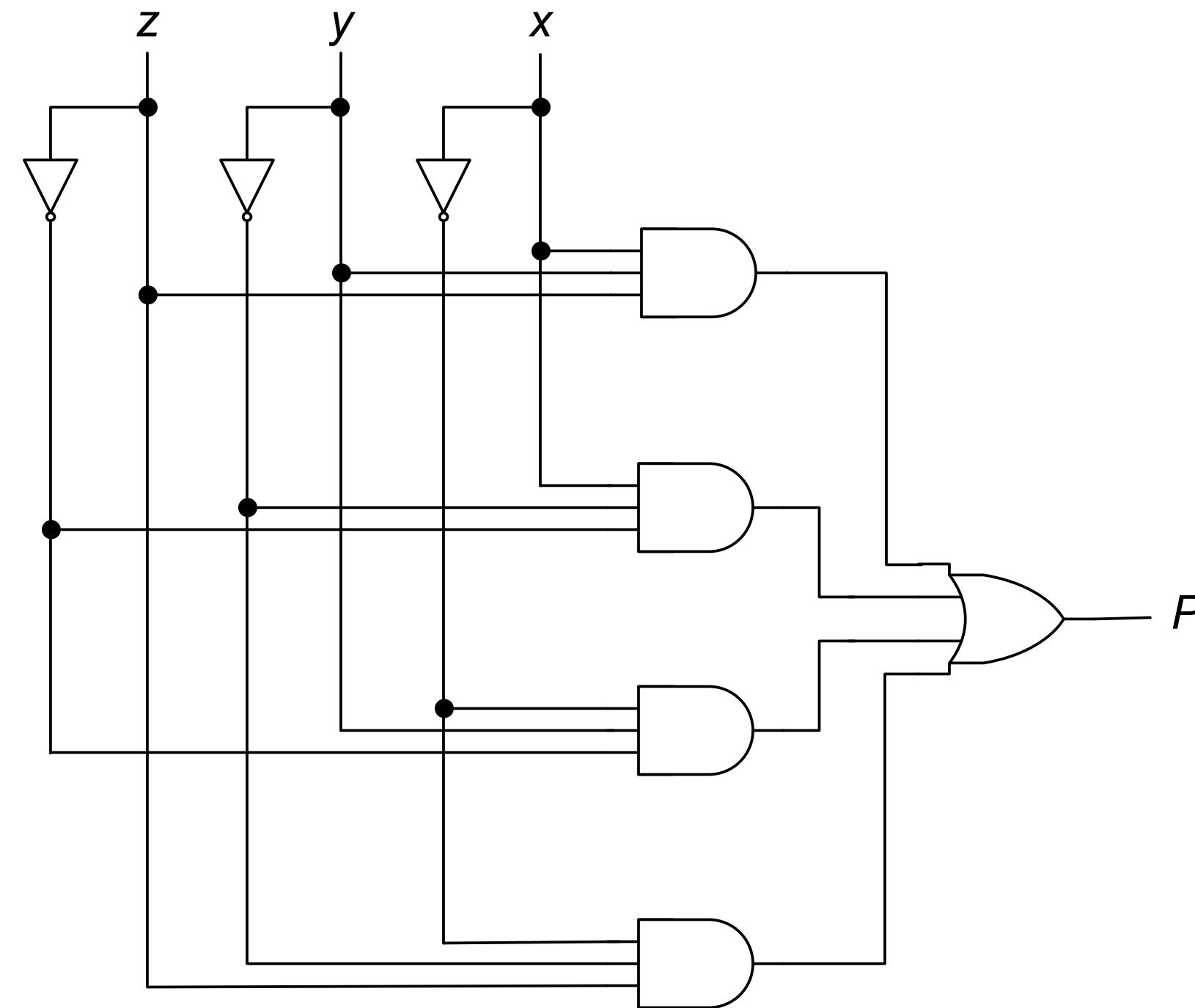


(b) Implementation.

$$P = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

Combinational Circuits: Serial to Parallel

Serial-to-parallel converter: distributes a sequence of binary digits on a serial input to a set of different outputs, as specified by external control signals


<i>Control</i>		<i>Output lines</i>				<i>Logic equations</i>
C_1	C_2	L_1	L_2	L_3	L_4	
0	0	x	0	0	0	$L_1 = xC_1' C_2'$
0	1	0	x	0	0	$L_2 = xC_1' C_2$
1	0	0	0	x	0	$L_3 = xC_1 C_2'$
1	1	0	0	0	x	$L_4 = xC_1 C_2$

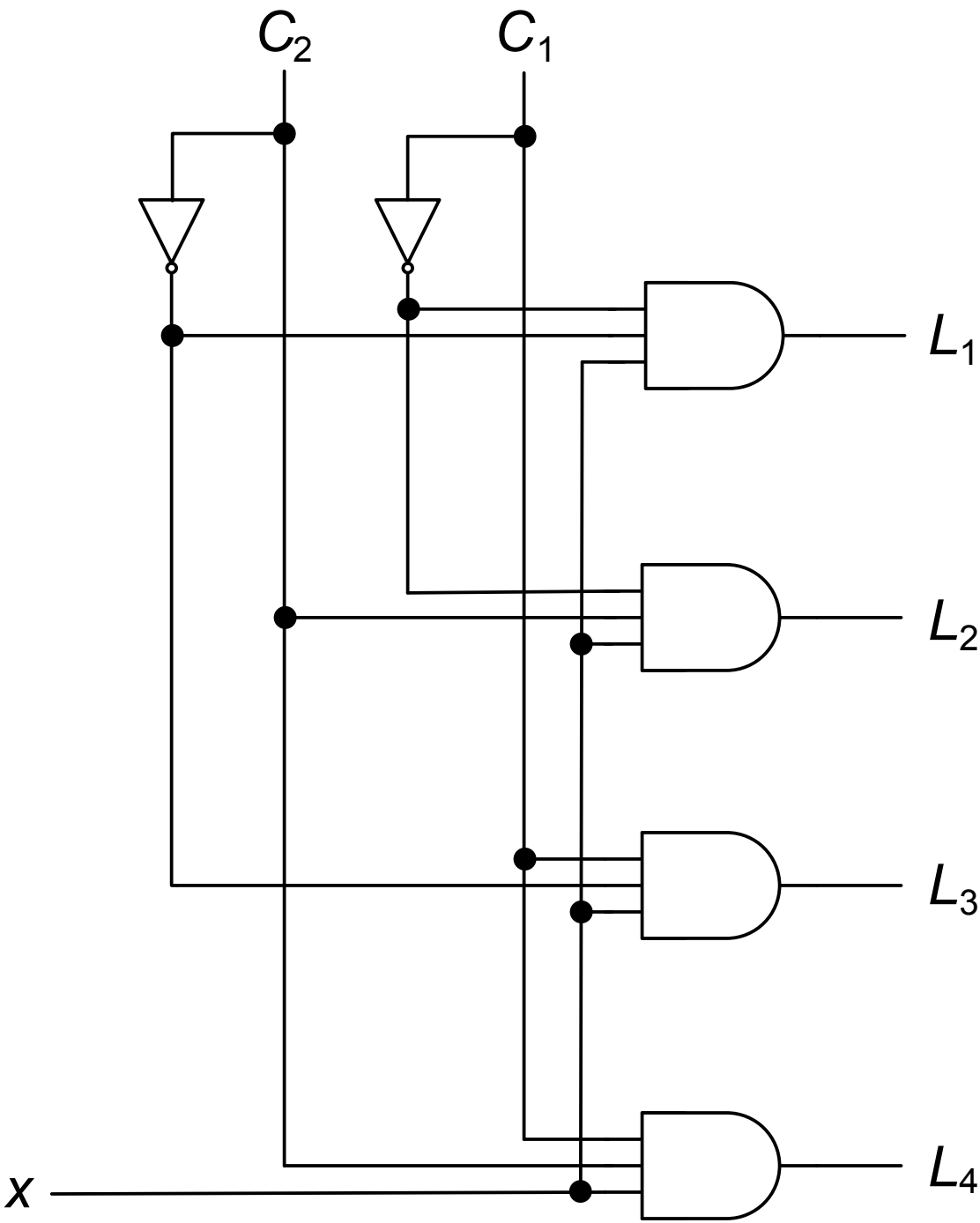

Combinational Circuits: Comparators

n -bit comparator: compares the magnitude of two numbers X and Y , and has three outputs f_1, f_2 , and f_3

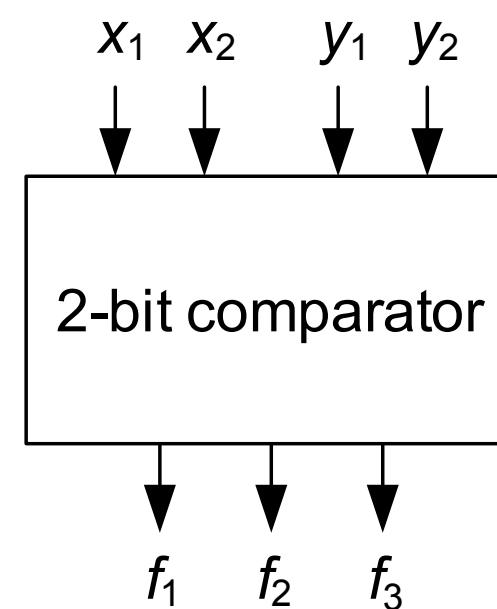- $f_1 = 1$ iff $X > Y$
- $f_2 = 1$ iff $X = Y$
- $f_3 = 1$ iff $X < Y$



(a) Block diagram.

$$f_1 = ?$$


$$f_2 = ?$$

$$f_3 = ?$$

Combinational Circuits: Comparators

n -bit comparator: compares the magnitude of two numbers X and Y , and has three outputs f_1, f_2 , and f_3

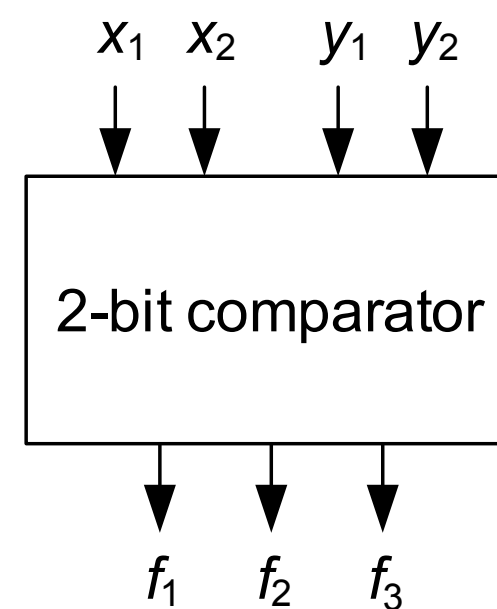- $f_1 = 1$ iff $X > Y$
- $f_2 = 1$ iff $X = Y$
- $f_3 = 1$ iff $X < Y$



(a) Block diagram.

$y_1y_2 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
y_1y_2	00	2	1	1	1
	01	3	2	1	1
	11	3	3	2	3
	10	3	3	1	2

(b) Map for f_1, f_2 , and f_3 .

$$f_1 = ?$$


$$f_2 = ?$$

$$f_3 = ?$$

Combinational Circuits: Comparators

n -bit comparator: compares the magnitude of two numbers X and Y , and has three outputs f_1, f_2 , and f_3

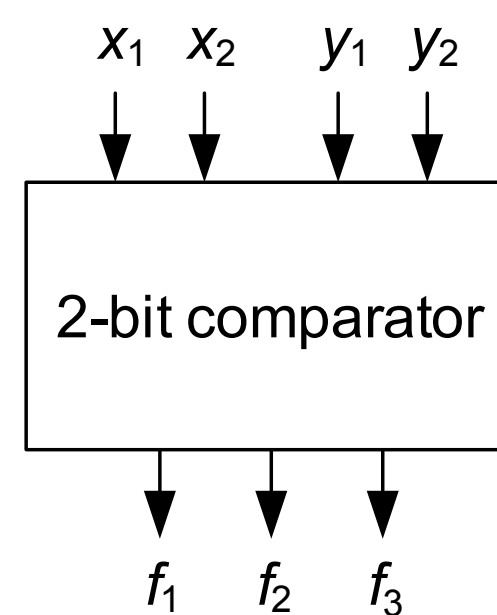
- $f_1 = 1$ iff $X > Y$
- $f_2 = 1$ iff $X = Y$
- $f_3 = 1$ iff $X < Y$



(a) Block diagram.

$x_1x_2 \backslash y_1y_2$		00	01	11	10
00	00	2	1	1	1
	01	3	2	1	1
	11	3	3	2	3
	10	3	3	1	2

(b) Map for f_1, f_2 , and f_3 .

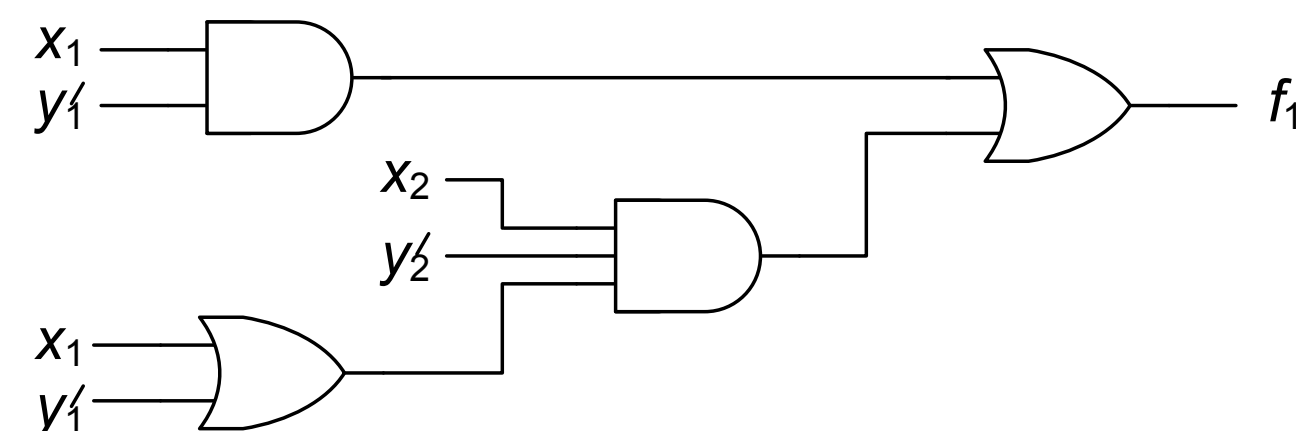

(c) Circuit for f_1 .

$$f_1 = x_1x_2y_2' + x_2y_1'y_2' + x_1y_1'$$

$$= (x_1 + y_1')x_2y_2' + x_1y_1'$$

$$f_2 = x_1'x_2'y_1'y_2' + x_1'x_2y_1'y_2 + x_1x_2'y_1y_2' + x_1x_2y_1y_2$$

$$= x_1'y_1'(x_2'y_2' + x_2y_2) + x_1y_1(x_2'y_2' + x_2y_2)$$

$$= (x_1'y_1' + x_1y_1)(x_2'y_2' + x_2y_2)$$

$$f_3 = x_2'y_1y_2 + x_1'x_2'y_2 + x_1'y_1$$

$$= x_2'y_2(y_1 + x_1') + x_1'y_1$$

Combinational Circuits: Comparators

Four-bit comparator: 8 inputs (four for A , four for B , and three outputs $A > B$, $A < B$ and $A = B$)

$$x_i = A_i B_i + A_i' B_i' \quad i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$


$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

Combinational Circuits: Multiplexers

Multiplexer: electronic switch that connects one of n inputs to the output

Data selector: application of multiplexer

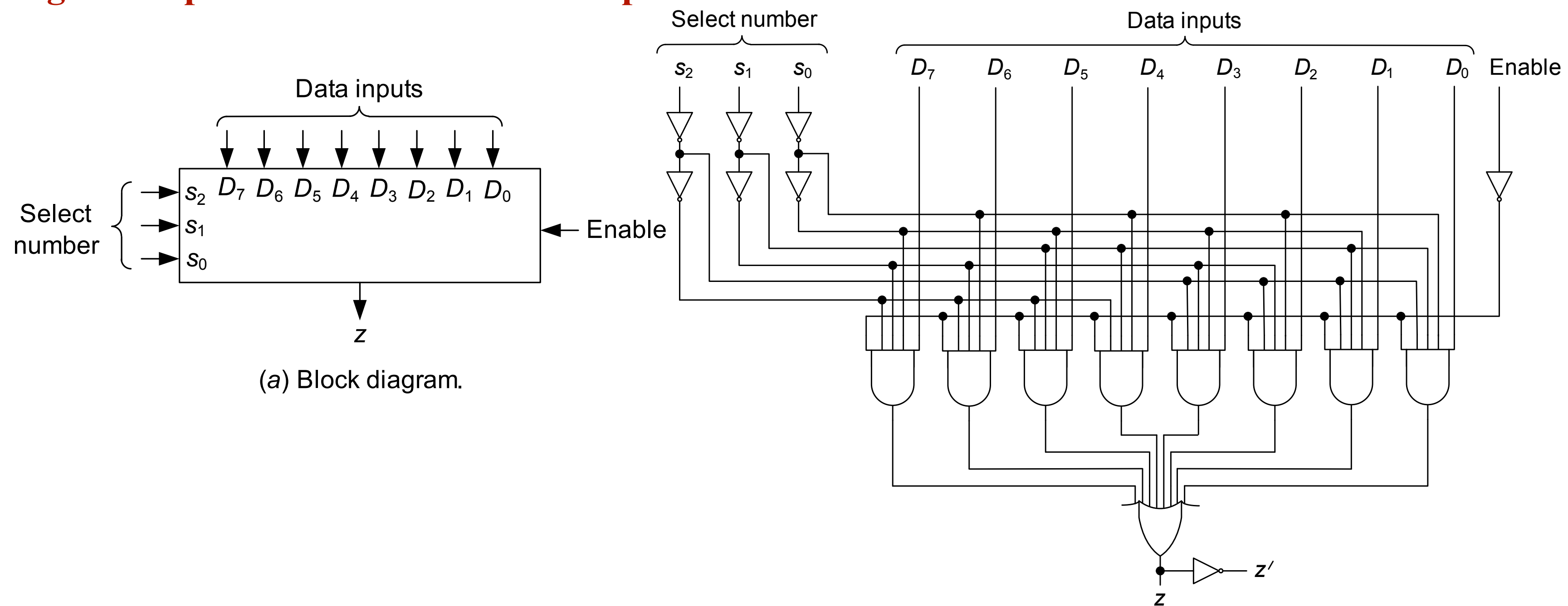- n data input lines, D_0, D_1, \dots, D_{n-1}
- m select digit inputs s_0, s_1, \dots, s_{m-1}
- 1 output
- **Can you design a simple data selectors with 2 input data lines?**




(b) Logic diagram.

Combinational Circuits: Multiplexers

Data selectors: can implement arbitrary switching functions

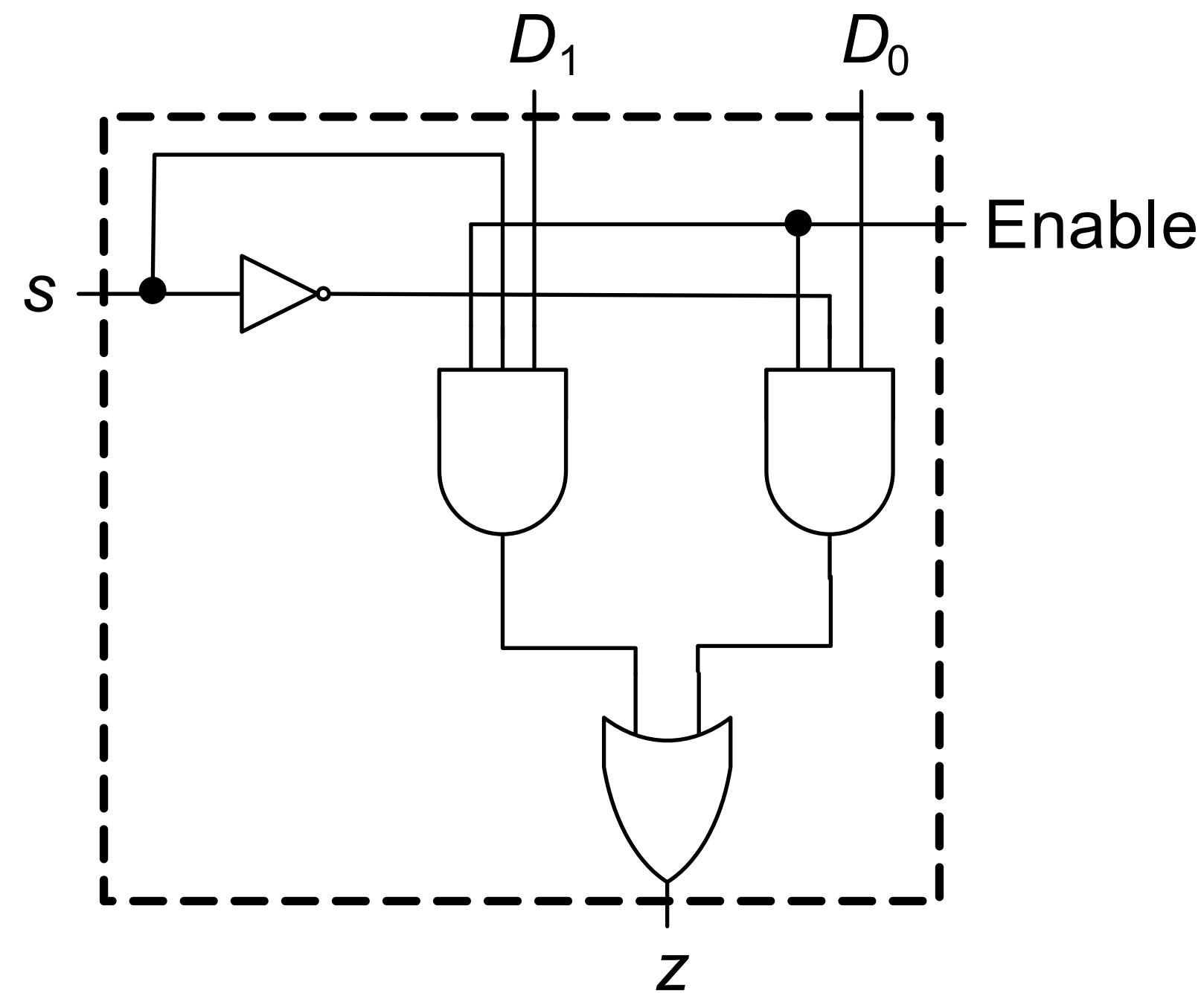Example: implementing two-variable functions



$$z = sD_1 + s'D_0$$

If $s = A$, $B = D_0$, and $B' = D_1$, then $z = A \oplus B$.

Implementing Switching Function with Mux

To implement an n -variable function: a data selector with $n-1$ select inputs and 2^{n-1} data inputs

Implementing three-variable functions:

$$z = s_2's_1'D_0 + s_2's_1D_1 + s_2s_1'D_2 + s_2s_1D_3$$

Example: $s_1 = A, s_2 = B, D_0 = C, D_1 = 1, D_2 = 0, D_3 = C'$

$$\begin{aligned} z &= A'B'C + AB' + ABC' \\ &= AC' + B'C \end{aligned}$$

General case: Assign $n-1$ variables to the select inputs and last variable and constants 0 and 1 to the data inputs such that desired function results